

EE Dept, IIT Bombay

Academic Year: 2024-2025, Semester II (Spring)

Course: MS101 Makerspace

EE Lecture 10

Transistors

Topics: (1) Transistor Basics, (2) BJT, (3) MOSFET, (4) Switches Using Transistors, (5) Logic Gates Using MOSFETs.

Reference: AS Sedra, KC Smith, TC Carusone, & V Gaudet, Microelectronic Circuits, 8th ed., Oxford University Press, 2020. Chs. 1, 2, 11, 13, 15.

1. Transistor Basics

Transistor

A transistor is a semiconductor device with three terminals, used in analog & digital applications.

It is mostly used as a 'two-port device' with one terminal common between the input and output ports.

Commonly used transistors

- Bipolar Junction Transistor (BJT)
- Metal Oxide Field Effect Transistor (MOSFET)


Both types are available as discrete devices and are used in analog and digital ICs.

Bipolar Junction Transistor (BJT): symbol & model

Types: NPN, PNP

Terminals: Emitter (E), Base (B), Collector (C)

*Circuit
symbol*

 


Two-port configurations with one terminal common between the input & output ports

- Common emitter (CE)
- Common base (CB)
- Common collector (CC)

Simplified small-signal model for CE configuration

(current-controlled current source)

 - Input: base current i_B
- Output: collector current $i_C = \beta i_B$
- β : Current gain




Metal Oxide Field Effect Transistor (MOSFET): symbol & model

Types

- N-channel enhancement mode
- P-channel enhancement mode
- N-channel depletion mode
- P-channel depletion mode

 *Circuit symbol
(enhancement
mode) with B-S
shorted*



Terminals: Source (S), Gate (G), Drain (D), Substrate / Body (B)


Two-port configurations with one terminal common between the input & output ports

- Common source (CS)
- Common gate (CG)
- Common drain (CD)


Simplified small-signal model for CS configuration

(voltage-controlled current source)

 - Input: gate-source voltage v_{GS}
- Output: drain current $i_D = g_m v_{GS}$
- g_m : trans-conductance
- $i_G \approx 0 \Rightarrow$ Almost no power from the input source.



 Some commercially available discrete transistor packages



2. Bipolar Junction Transistor (BJT)

NPN transistor


Emitter (E): heavily doped N region

Base (B) : very thin P region

Collector (C): lightly doped N region

Active mode operation

 - BE junction is forward biased.
- BC junction is reversed biased.



Source: Fig 6.3:-Sedra A S, Smith K C, "Microelectronic Circuits", Oxford University Press, 7Ed. ISBN: 9780199339136

Active mode operation: a cricket analogy

- The emitter is the bowler who shoots balls (electrons) toward the base.
- The base is the batsman, a tail-ender who swings away but connects with only 1-2% of the incoming balls (electrons).
- Most of the balls (electrons) are collected by the wicketkeeper (collector).

Current relations


KCL: $I_E = I_B + I_C$

Transistor action

$$\Delta I_C = \alpha \Delta I_E \quad (\alpha \approx 0.90 - 0.99)$$

$$\Delta I_C = \beta \Delta I_B$$

 $I_C = \beta I_B$ is used as an approximate relation.



Relation between α & β


$$\Delta I_E = \Delta I_B + \Delta I_C \Rightarrow \Delta I_B = \Delta I_E - \Delta I_C = (1/\alpha - 1) \Delta I_C$$

$$\Rightarrow \Delta I_C = \alpha / (1 - \alpha) \Delta I_B = \beta \Delta I_B$$

$$\Rightarrow \beta = \alpha / (1 - \alpha)$$


$$\text{Example: } \alpha = 0.98 \Rightarrow \beta = 0.98 / 0.02 = 49$$

 NPN transistor characteristics: I_C vs V_{CE}



Operation states

 - Active: Forward biased BE junction, reverse biased BC junction.
- ON (saturation): Forward biased BE & BC junctions. High I_B , High I_C , Low V_{CE} .
- OFF (cutoff): Reverse biased BE & BC junctions. $I_B \approx 0$, $I_C \approx 0$, High V_{CE} .



NPN transistor as a switch

Common emitter (CE) configuration

- Control input on the base side
- Load on the collector side
- ON / OFF control by changing the base current I_B

OFF: $V_{BE} < V_\gamma$

BE junction cutin voltage: $V_\gamma \approx 0.5 \text{ V}$

$I_B \approx 0$, $I_C \approx 0$, $V_{CE} \approx V_{CC}$

$V_{BC} < 0$


Heavily ON: $I_B > I_C / \beta$

$V_{BE} = V_{BES}$, $V_{CE} = V_{CES}$

Saturation voltages: $V_{BES} \approx 0.8 \text{ V}$, $V_{CES} \approx 0.2 \text{ V}$

$I_C = (V_{CC} - V_{CES}) / R_L$

$V_{BC} > 0$

 

3. Metal Oxide Semiconductor Field Effect Transistor (MOSFET)


Types

- N-channel enhancement-mode
- P-channel enhancement-mode
- N-channel depletion-mode
- P-channel depletion-mode


Terminals: Source (S), Gate (G), Drain (D), Substrate / Body (B)

Commonly used MOSFETs: N-channel & P-channel enhancement-mode


N-channel
enhancement-mode
MOSFET

 

 Enhancement-mode device symbols
(B-S usually shorted in switching & logic circuits)




P-channel
enhancement-mode
MOSFET

 


Operation: Voltage-controlled current source device. Gate-source voltage (V_{GS}) controls drain current (I_D).
Nearly zero gate current (I_G) \Rightarrow Almost no power taken from the input source.

 N-channel enhancement-mode MOSFET operation




 - The D & S terminals are interchangeable, with $V_{DS} > 0$.
- No D-S channel is available at $V_{GS} = 0$.
- For N-channel, the D-S channel is formed for $V_{GS} > V_T$ (threshold voltage > 0)
- OFF-state: $V_{GS} < V_T$. Very high resistance for drain-source current flow.
- ON-state: $V_{GS} > V_T + \text{a few V}$. Low resistance for drain-source current flow.




MOSFET Type	Condition for Switching
N-channel Enhancement	OFF for $V_{GS} < V_T$ (0.6 to 1 V)
P-channel Enhancement	OFF for $V_{GS} > V_T$ (−1.0 to 0.6 V)

 N-channel enhancement-mode MOSFET characteristics: I_D vs V_{DS}




- $V_{DS} > 0$. D-S conduction starts when the N-channel is formed between the D & S terminals.
- V_T is the minimum value of V_{GS} for the channel formation. Channel is formed for $V_{GS} > V_T$. Channel resistance decreases as V_{GS} increases further.
- OFF state: $V_{GS} < V_T$, $I_G \approx 0$, $I_D \approx 0$, $V_{DS} \approx V_{DD}$
- ON state: $V_{GS} > V_T + \text{a few V}$
 $I_G \approx 0$, $V_{DS} \approx 0$, $I_D \approx V_{DD} / R_L$

 

Typical ' V_{DS} - I_D ' characteristics for N channel Enhancement mode MOSFET
A & B: operating points for switching action

4. Switches Using Transistors


BJT switch with V_{in} as control

 

BJT switch for load R_L connected to +ve supply end (V_{CC})

- Control input V_{in}
- NPN BJT in common-emitter (CE) configuration
- R_B for limiting I_B
- OFF: $I_B \approx 0$ ($V_{in} = \text{low}$)
- ON: $I_B > I_C/\beta$ ($V_{in} = \text{high}$)

MOSFET switch with V_{in} as control

 


MOSFET switch for load connected to +ve supply end (V_{DD})

- Control input V_{in}
- N-channel MOSFET in common-source (CS) configuration
- R_1 and R_2 for voltage attenuation, if V_{in} -peak is large
- OFF: $V_{GS} < V_T$ ($V_{in} = \text{low}$)
- ON: $V_{GS} > V_T + \text{a few V}$ ($V_{in} = \text{high}$)


For load R_L connected to -ve supply end, we use PNP BJT in CE configuration or P-channel MOSFET in CS configuration.

NPN BJT Switch Operation

 

NPN BJT switch

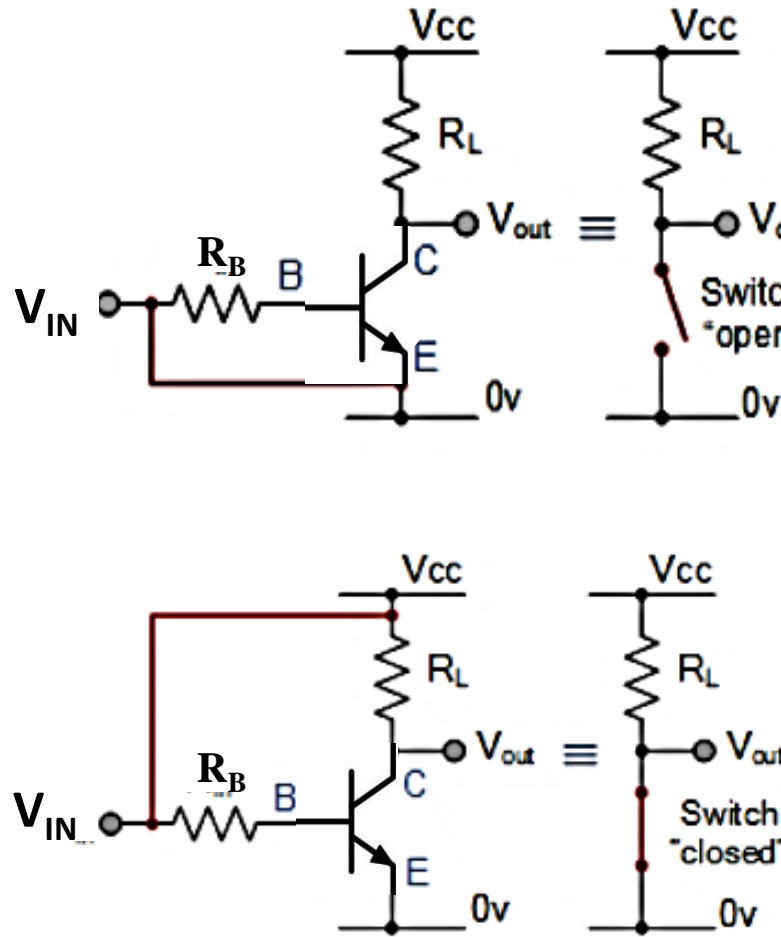Control input V_{IN} , with binary levels 0 & V_{CC}




(a) $V_{IN} = 0$

- $V_{BE} = 0 < 0.5$ V.
- BJT operates as open switch.
 $I_B \approx 0$, $V_{CE} \approx V_{CC}$, $I_C \approx 0$.
- BE junction is not forward biased.
- BC junction is reverse biased.

(b) $V_{IN} = V_{CC}$


- BE junction is forward biased. I_B is limited by R_B . V_{BE} reaches saturation value $V_{BES} (\approx 0.8$ V).
- Collector voltage drops until BC junction gets forward biased. V_{CE} reaches saturation value $V_{CES} (\approx 0.2$ V).
- BJT operates as closed switch.
- $V_{BE} = 0.8$ V. $V_{out} = V_{CES} = 0.2$ V.
 $I_B = (V_{CC} - 0.8) / R_B$.
 $I_C = (V_{CC} - V_{CES}) / R_L$.

N-channel MOSFET Switch Operation

 

N-channel MOSFET switch

 Control input V_{IN} , with binary levels 0 & V_{DD} . Usually R_1 is short and R_2 is open.



Let $V_{DD} = 12\text{ V}$, $V_T = 2\text{ V}$, $R_1 = 0$, $R_2 = \infty$.

(a) $V_{in} = 0$

- $V_{GS} = 0 < V_T$
- MOSFET operates as open switch.

$$I_G \approx 0$$

$$V_{DS} \approx V_{DD}$$

$$I_D \approx 0.$$

(b) $V_{in} = V_{DD}$

- $V_{GS} = 12\text{ V} > V_T$
- MOSFET operates as closed switch.


$$I_G \approx 0$$

$$V_{DS} \approx 0$$

$$I_D = V_{DD}/R_L$$

NPN and PNP BJT Switches for LED Control

 NPN switch for load connected to +ve supply end (V_{cc})



Given: $V_{cc} = 5\text{ V}$. V_{in} (LED off) = 0 V. V_{in} (LED on) = 5 V.
 $\beta > 50$. I_L (full brightness) = 10 mA. LED voltage drop = 2 V.

$$I_L = (V_{CC} - V_{LED} - V_{CES}) / R_2 = (5 - 2 - 0.2) / R_2 > 10\text{ mA}$$

$$\Rightarrow R_2 < 2.8 / 10\text{ k}\Omega = 280\ \Omega.$$


$$\text{Let } R_2 = 270\ \Omega. \Rightarrow I_L = 10.3\text{ mA}.$$

$$I_B = [(V_{in})_{\text{high}} - V_{BES} - 0] / R_1 > I_L / \beta_{\text{min}}$$

$$\Rightarrow (5 - 0.8 - 0) / R_1 > 10.3 / 50 \Rightarrow R_1 < 20.38\text{ k}\Omega.$$

$$\text{Let } R_1 = 18\text{ k}\Omega.$$

 PNP switch for load connected to -ve supply end (GND)



Given: $V_{cc} = 5\text{ V}$. V_{in} (LED off) = 5 V. V_{in} (LED on) = 0 V.
 $\beta > 50$. I_L (full brightness) = 10 mA. LED voltage drop = 2 V.

$$I_L = [V_{CC} - V_{ECS} - V_{LED}] / R_2 = [5 - 0.2 - 2] / R_2 > 10\text{ mA}$$

$$\Rightarrow R_2 < 2.8 / 10\text{ k}\Omega = 280\ \Omega.$$


$$\text{Let } R_2 = 270\ \Omega, \Rightarrow I_L = 10.3\text{ mA}.$$

$$I_B = [V_{CC} - V_{EBS} - (V_{in})_{\text{low}}] / R_1 > I_L / \beta_{\text{min}}$$

$$\Rightarrow (5 - 0.8 - 0) / R_1 > 10.3 / 50 \Rightarrow R_1 < 20.38\text{ k}\Omega.$$

$$\text{Let } R_1 = 18\text{ k}\Omega.$$

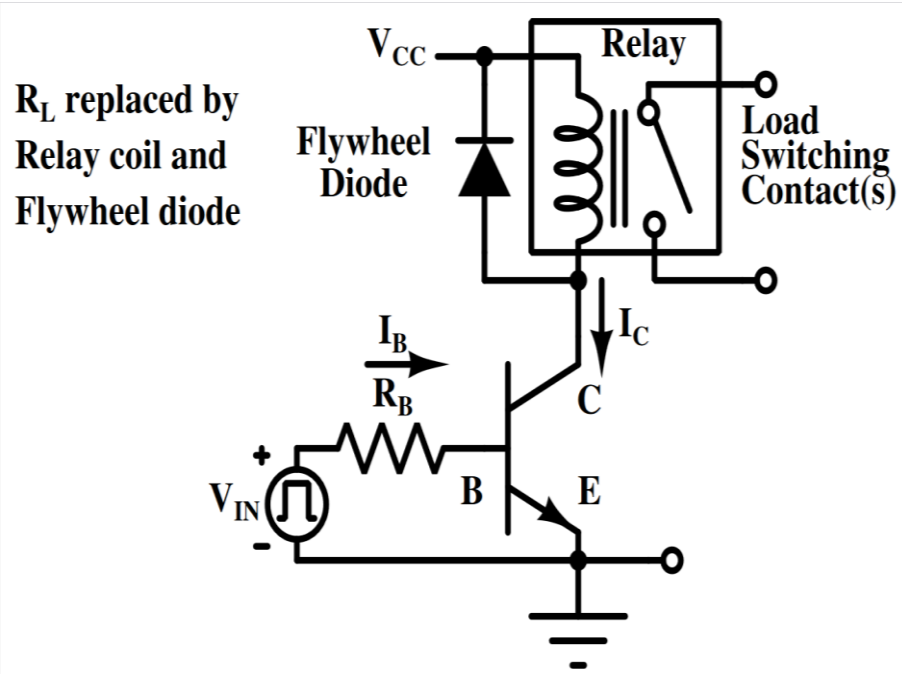BJT Switch for Electromagnetic Relay Control




Relay Symbols



- Relay is used for switching loads with large voltage & current and for electrical isolation of the control circuit from the load voltage.
 - The relay coil has a resistance and an inductance. It is activated if the coil current is above a certain threshold.
 - Turning off the coil current generates a large voltage at its lower end (i.e. collector terminal). To protect the transistor from high V_{CE} , “flywheel diode” is used. When the transistor is turned off, the diode turns on, limiting V_{CE} to $V_{CC} + V_D$. The coil current slowly decays to zero.
-
- NPN transistor for relay connected to +ve supply.
 - The relay coil current (I_C) is switched by controlling the transistor base current (I_B). Transistor current Gain $\beta = I_C / I_B$.
 - Load switching contacts of the relay switch the load with large voltage & current.
 - The relay control circuit is electrically isolated from the load.

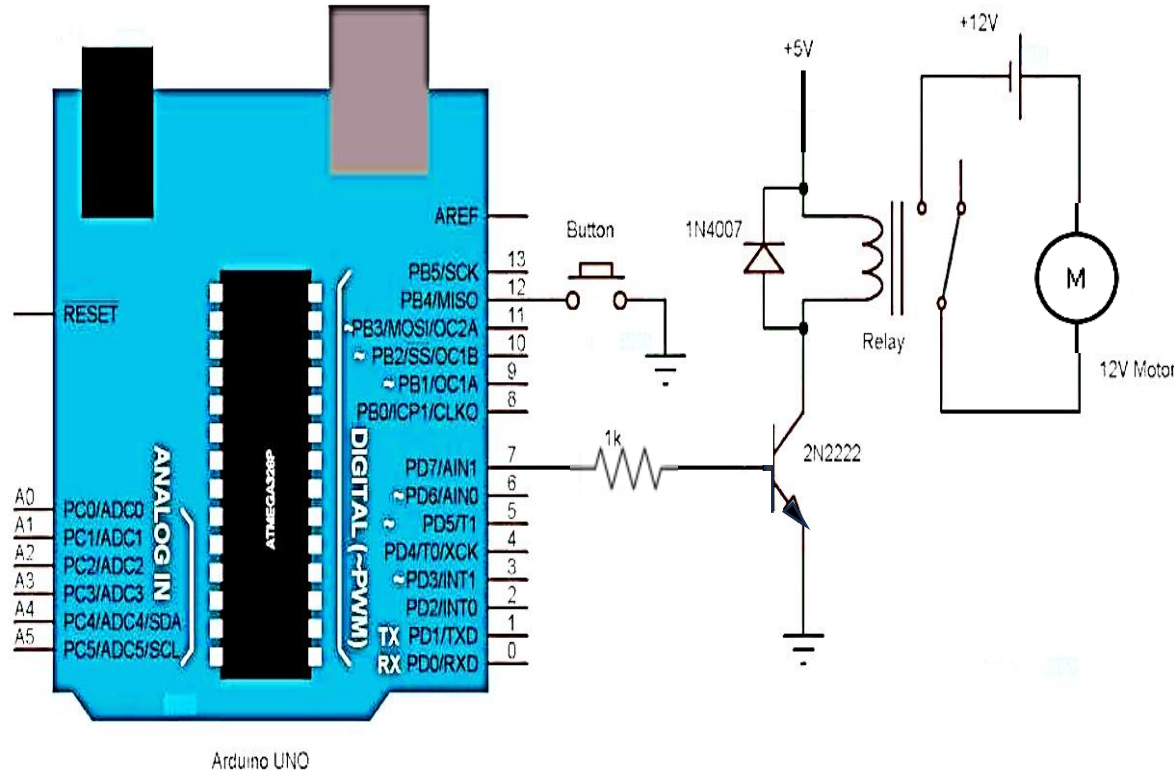Relay Switching Using Micro-Controller (Arduino)



Arduino Relay Control Circuit Diagram

Example

Control of a relay with 'Arduino' digital output pin PD7 and NPN transistor 2N2222.

Relay coil current = 60 mA.

Transistor $\beta_{\min} = 30$.

Set the pin PD7 to 'Hi'. It will put the transistor in ON state, allowing current to flow through the relay coil making the relay ON.

$I_B > \text{Relay current} / \beta_{\min} = 2 \text{ mA}$.

Diode is connected in parallel with the relay coil to avoid sudden change of current in it and thereby to avoid large voltage at the transistor's collector terminal.

Source: <https://www.electronicshub.org/arduino-relay-control/>

5. Logic Gates Using MOSFETs



Complementary Metal Oxide Semiconductor (CMOS) Circuits

1. Combination of N-channel and P-channel MOSFETs
2. Usually same gate signal goes to N-channel and its complementary P-channel transistors for logic circuits
3. Negligible steady-state power consumption in CMOS digital circuits


Some CMOS Logic Gates

- CMOS Inverter
- CMOS NAND Gate – Universal gate
- CMOS NOR Gate – Universal Gate
- CMOS Tri-state Inverter

CMOS Inverter

  


Ideal Digital Operation

 

Practical Inverter Characteristics


CMOS 2-Input NAND Gate

 

TRUTH TABLE

TRUTH TABLE			STATE OF THE TRANSISTORS			
A	B	Y	NMOS1	PMOS1	NMOS2	PMOS2
0	0	1	OFF	ON	OFF	ON
0	1	1	OFF	ON	ON	OFF
1	0	1	ON	OFF	OFF	ON
1	1	0	ON	OFF	ON	OFF

CMOS 2-Input NOR GATE

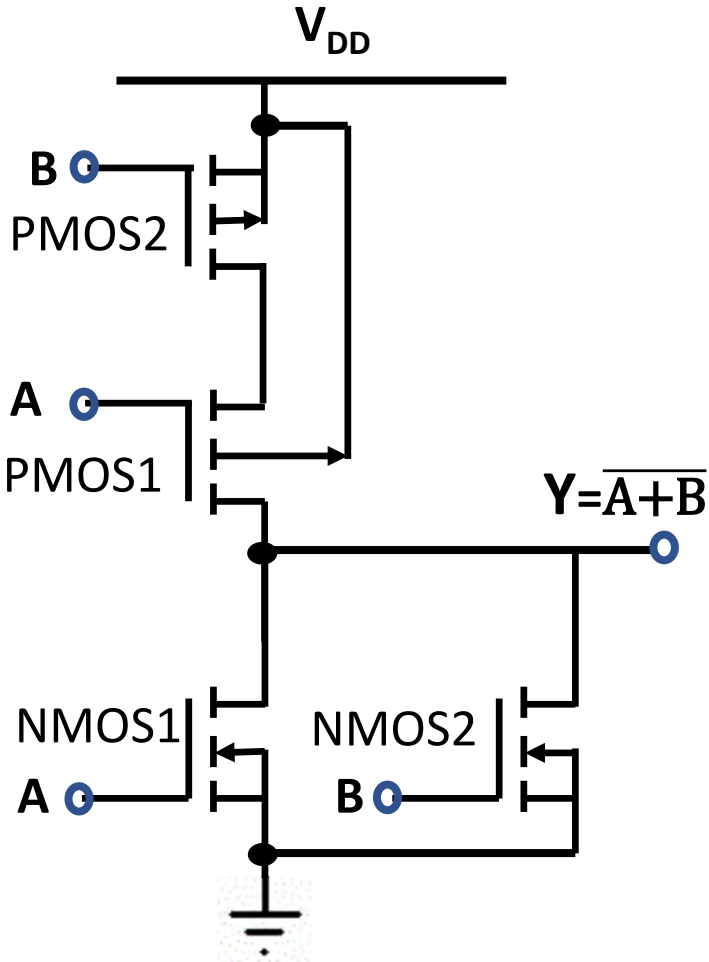


TRUTH TABLE

A	B	Y	NMOS1	PMOS1	NMOS2	PMOS2
0	0	1	OFF	ON	OFF	ON
0	1	0	OFF	ON	ON	OFF
1	0	0	ON	OFF	OFF	ON
1	1	0	ON	OFF	ON	OFF

STATE OF THE TRANSISTORS

CMOS Tri-state Inverter

 

- When $EN=1$, $V_{OUT} = \overline{V_{IN}}$
- When $EN=0$, V_{OUT} is in the high impedance state

* * * * *